
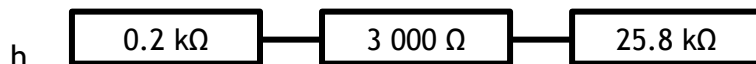
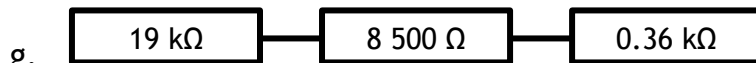
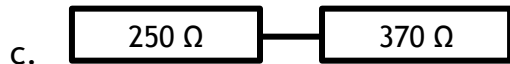


Task 1



Determine the total resistance in the following arrangements.





$$R_{\text{TOTAL}} = R_1 + R_2$$

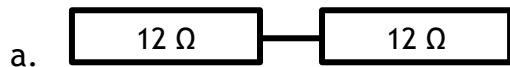

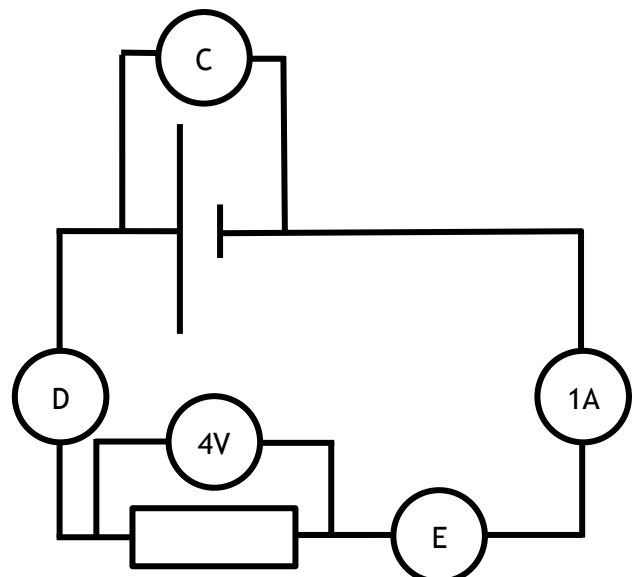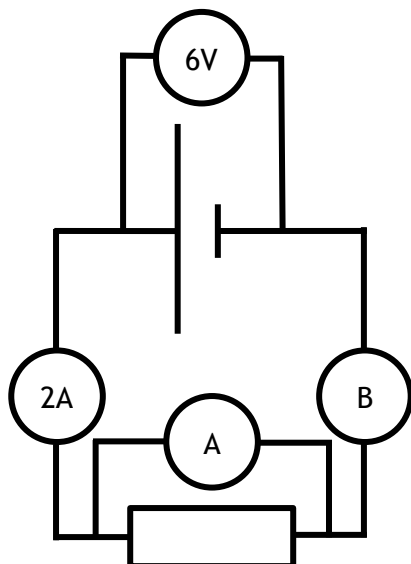Task 2

Look at these diagrams. Decide whether the meters A-Y are voltmeters or ammeters. What are the readings on each meter (include the units)?



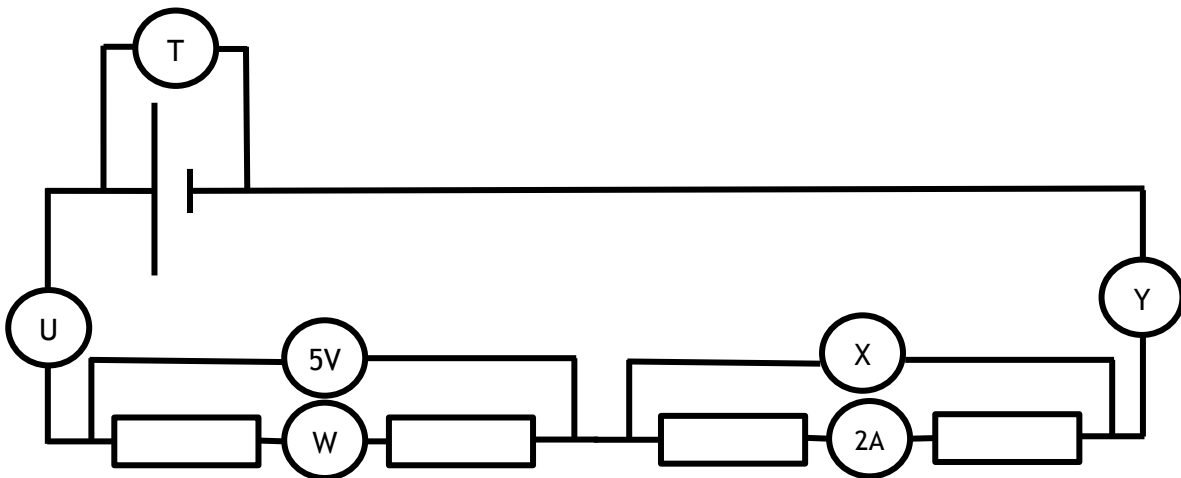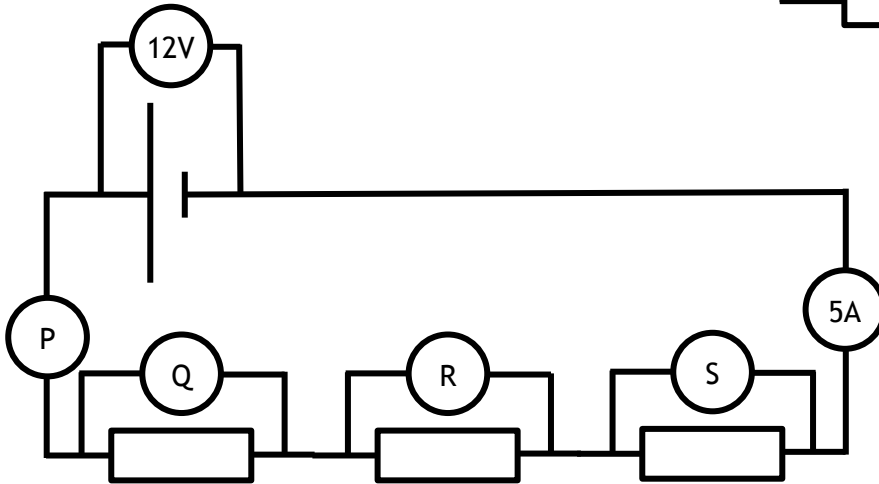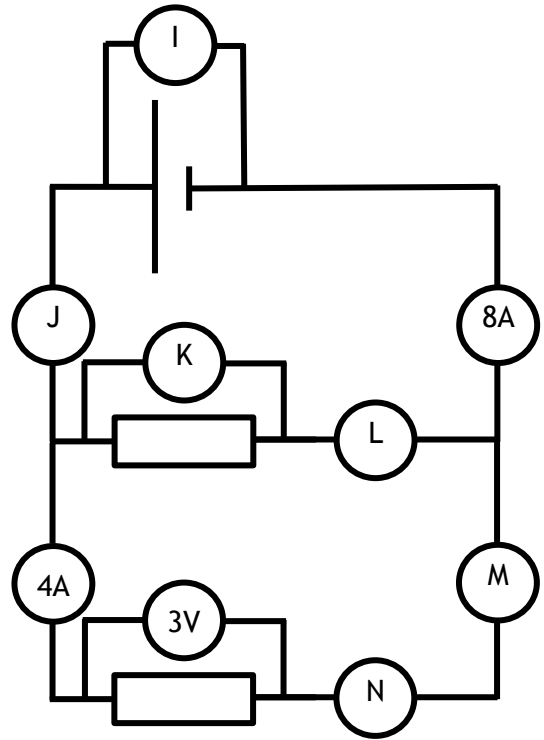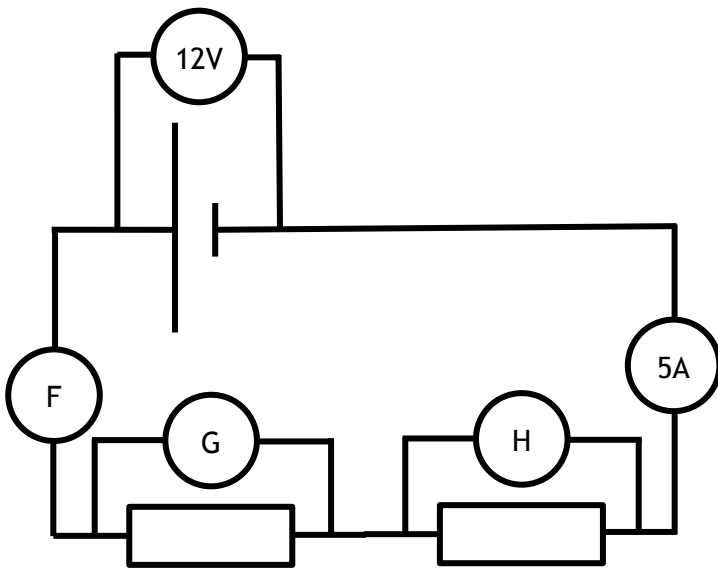

## Answers

1.

- |                    |                     |
|--------------------|---------------------|
| a. $24 \Omega$     | f. $1\,630 \Omega$  |
| b. $120 \Omega$    | g. $27\,860 \Omega$ |
| c. $620 \Omega$    | h. $29\,000 \Omega$ |
| d. $148 \Omega$    | i. $24\,900 \Omega$ |
| e. $6\,800 \Omega$ | j. $16\,938 \Omega$ |

2.

- |                  |                   |
|------------------|-------------------|
| A. Voltmeter 6 V | N. Ammeter 4 A    |
| B. Ammeter 2 A   | O. -              |
| C. Voltmeter 4 V | P. Ammeter 5 A    |
| D. Ammeter 1 A   | Q. Voltmeter 4 V  |
| E. Ammeter 1 A   | R. Voltmeter 4 V  |
| F. Ammeter 5 A   | S. Voltmeter 4 V  |
| G. Voltmeter 6 V | T. Voltmeter 10 V |
| H. Voltmeter 6 V | U. Ammeter 2 A    |
| I. Voltmeter 3 V | V. -              |
| J. Ammeter 8 A   | W. Ammeter 2 A    |
| K. Voltmeter 3 V | X. Voltmeter 5 V  |
| L. Ammeter 4 A   | Y. Ammeter 2 A    |
| M. Ammeter 4 A   |                   |